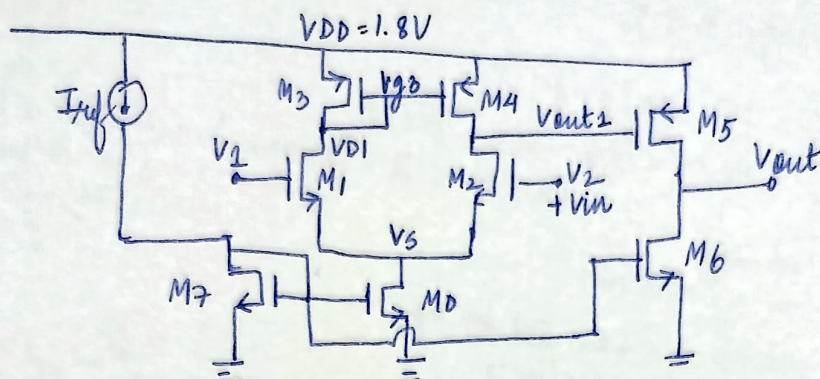


(i) Circuit diagram :


$$\rightarrow I_{ref} = 4.25 \mu A$$

$$V_{OV_7} = V_{GS_7} - V_{th_7}$$

$$\rightarrow V_{0V,7} = 0.09V$$

* Based on the initial assumptions as stated above,

$$\left(\frac{W}{L}\right)_7 = \frac{2 I_{ref}}{K_n(\text{ox})(V_{ov7})^2} = \frac{2 \times 4.25 \times 10^{-4}}{230 \times 81} \approx 4.5 \quad \begin{matrix} (L = 900 \text{ nm}) \\ (W = 3600 \text{ nm}) \end{matrix}$$

∴ The tail current of the OTA is designed to be 10 times of the reference I_{ref} ,
($W = 3600 \text{ nm}$)

$$\left(\frac{W}{L}\right)_0 = 10 \left(\frac{W}{L}\right)_7 = 45 \quad \begin{matrix} L = 900 \text{ nm} \\ W = 40500 \text{ nm} \end{matrix}$$

* For M_0 to be in saturation: $V_S > (V_{GS} - V_{th})_0 \Rightarrow V_S > 0.09V$

* For saturation: $V_S > (V_{GS} - V_{th})_0 \Rightarrow V_S > 0.09V$
 * For the current to split equally at node S, $(\frac{W}{L})_{M1} = (\frac{W}{L})_{M2} = \frac{1}{2} (\frac{W}{L})_0 = 22.5$
 Thus, $W_1 = W_2 = 20250 \text{ nm}$; $L_1 = L_2 = 900 \text{ nm}$

NOTE

$$* V_{gs1} - V_{th1} = 0.09V$$

$$\Rightarrow 0.9 - V_S - 0.37 = 0.09 \Rightarrow V_S = 0.44 \text{ V} > 0.09 \text{ V}$$

(\therefore Mo is in saturation)

* For M_1 to be saturation, $V_{D1} > V_{gs2} - V_{th1} > 0.09V$

* For M_3 and M_4 , $I_3 = I_4 = 21.25 \text{ pA}$

$$I_3 = \frac{\mu p \cos}{2} \times \left(\frac{W}{L}\right)_3 \times (V_{sg} - |V_{tp}|)_3$$

$I_3 = \frac{\mu p C_{ox}}{2} \times \left(\frac{W}{L}\right)_3 \times (V_{sg} - |V_{tp}|)_3$
 + Assume $\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 3.5 \Rightarrow (V_{sg} - |V_{tp}|)_3 = 0.372 \text{ V}$

Thus, $w_3 = w_4 = 3150 \text{ nm} \approx 3200 \text{ nm}$ (for the sake of simplicity in calculations)
 $L_3 = L_4 = 900 \text{ nm}$ $|V_{4p}| = 0.39 \text{ V}$

Thus, $W_3 = W_4 = 3150 \text{ nm}$
 $L_3 = L_4 = 900 \text{ nm}$
 For M_3 to be on, $V_{sg3} > |V_{tp}|_3 \Rightarrow 1.8 - |V_{tp}| > V_{g3}$ ($|V_{tp}| = 0.39 \text{ V}$)
 $V_{g3} < 1.41 \text{ V}$

$$(V_{sg} - |V_{tp}|)_3 = 0.372 \Rightarrow 1.8 - 0.372 - 0.39 - |V_{D1}| = 0.372$$

$\Rightarrow V_{D1} = 1.038 \text{ V}$ and M_a are in satⁿ.

$\Rightarrow |V_1| = 1.058 \text{ V}$
Thus, even M_3 and M_4 are in satⁿ.

Thus, even M_3 and M_4 are in sat.

The above theoretical calculations require modifications due to presence of non-idealities such as channel length modulation and body effect.

3.27

$$\left(\frac{W}{L}\right)_7 = \frac{3400 \text{ nm}}{900 \text{ nm}} \approx 3.77$$

The first stage gain may be calculated using the values from the log file attached.

$$|A_{v1}| = \frac{|v_{out1}|}{v_{in}} = g_{m2} (r_{on2} || r_{op4})$$

$$|A_{v1}| = \frac{4.03 \times 10^{-4}}{4} (343,642 || 952,380)$$

$$|A_{v1}| = 101.76$$

As per simulation, $|A_{v1}| = 101.23$
 \therefore error is nearly 0.5%

* For M6:

Assume $I_6 = 25.5 \mu A$

Then, since, $(V_{gs} - V_{th})_6 = (V_{gs} - V_{th})_0 = 0.09V$

$$\left(\frac{W}{L}\right)_6 = \frac{2 I_6}{\mu_n C_{ox} (V_{gs} - V_{th})_6^2}$$

$= 22.04 \approx 20$ (approximated due to practical considerations pertaining to non-idealities)

$\therefore W = 20000 \text{ nm}$, $L = 900 \text{ nm}$

Practical observation of $I_6 = 24.48 \mu A$

Also $V_{out} > (V_{gs} - V_{th})_6 \Rightarrow V_{out} > 0.09V$

* For M5:

$$(V_{sg} - |V_{tp}|)_5 = V_{gs} - V_{out1} - |V_{tp}| \quad (V_{gs} - V_{out1}) - |V_{tp}|$$

where $V_{out1} = 906.98 \text{ mV} = 0.9V$, but theoretical = $1.038V$ (as calculated earlier)

$$\therefore V_{sg} - |V_{tp}|_5 = 1.8 - 0.9 - 0.39 = 1.8 - 1.038 - 0.39$$

$$= 0.372V$$

$$I_5 = I_6 = 25.5 \mu A$$

$$\therefore 25.5 \times 10^{-6} = \frac{100 \times 10^{-6}}{2} \times \left(\frac{W}{L}\right)_5 \times (0.372)^2$$

$$\left(\frac{W}{L}\right)_5 = 3.71$$

Using $V_{sd} > V_{sg} - |V_{tp}|_5 \Rightarrow V_{out} = 0.9V$

Thus, M5 and M6 both are in saturation

* Second stage gain

$$|A_{v2}| = g_{m5} \times (r_{op5} || r_{on6})$$

$$= 9.4 \times 10^{-5} \times (840336.13 || 381,679.38)$$

$$= 24.67$$

\therefore Overall voltage gain for open loop OTA

$$|A_{v3}| = |A_{v1}| |A_{v2}|$$

$$|A_{v1}| = 101.76 \times 24.67$$

$$|A_{v1}| = 2510.61$$

Practically,

$$|A_{v1}| = 101.23$$


$$|A_{v2}| = 26.71$$

$$\therefore |A_{v1}| = |A_{v1}| |A_{v2}|$$

$$= 2703.3$$

$$\therefore \text{error} = 7.4\%$$

II) CLOSED LOOP CONFIGURATION

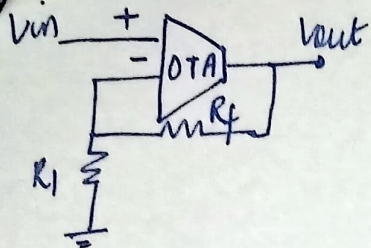

$$V_{out} = A(V_+ - V_-)$$

Consider ∞ gain, $V_+ = V_-$

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_1}$$

For gain = 2, $R_f = R_1 = 20k\Omega$

However, the OTA I designed has $A \neq \infty$ ($A = 2550$)

$$\therefore V_{out} - AV_{in} = -AV_-$$

$$\Rightarrow V_- = \frac{AV_{in} - V_{out}}{A}$$

KCL at V_- yields:


$$\frac{AV_{in} - V_{out}}{A} - \frac{V_{out}}{R_f} = \frac{V_{out} - AV_{in}}{AR_1}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A(R_1 + R_f)}{(A+1)R_1 + R_f}$$

Choose $R_f = 22.5k\Omega$ and $R_1 = 20k\Omega \Rightarrow \frac{V_{out}}{V_{in}} = 2.124$

Practically, $\frac{V_{out}}{V_{in}} = 2.18$

Circuit diagram:

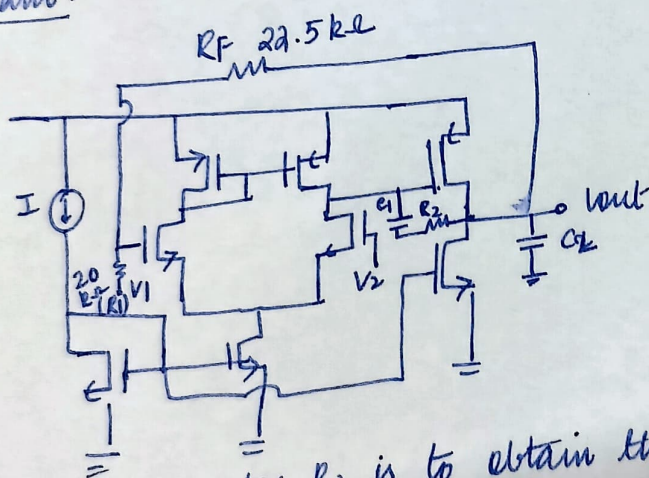

$$V_1 = 0.9V$$

$$V_2 = 0.9V + 0.0001 \sin(2000\pi t)$$

$$C_1 = 3pF, C_2 = 10pF$$

The purpose of the resistor R_2 is to obtain the required phase margin ($60^\circ - 70^\circ$).
Choosing a suitable R_2 is important so as to fix the P.M at 60°
 $\therefore R_2 = 9.6k\Omega$

$$3dB \text{ bandwidth} = 12.974 MHz$$

$$\text{Location of dominant pole} = \frac{1}{A_{V2} \times C_1 \times (10p51111006)}$$

$$= \frac{1}{24.61 \times 3 \times 10^{-12} \times (840336 \times 381679)}$$

$$= 0.0422 \times 52,295.86 s^{-1}$$

$$\begin{aligned} \text{Power dissipation} &= V_{DD} \times (I_{D7} + I_{D5} + I_{D3} + I_{D4}) \\ &= 1.8 \times (4.25 + 42.5 + 24.48) \times 10^{-6} \\ &= 128.86 \mu W \end{aligned}$$

Theoretical:

$$(i) \left(\frac{W}{L}\right)_7 = 4.5$$

$$(ii) \left(\frac{W}{L}\right)_0 = 45$$

$$(iii) \left(\frac{W}{L}\right)_1 = 22.5$$

$$(iv) \left(\frac{W}{L}\right)_2 = 22.5$$

$$(v) \left(\frac{W}{L}\right)_3 = 3.5$$

$$(vi) \left(\frac{W}{L}\right)_4 = 3.5$$

$$(vii) \left(\frac{W}{L}\right)_5 = \cancel{22} 3.7$$

$$(viii) \left(\frac{W}{L}\right)_6 = 22$$

$$(ix) \text{ Stage -1 gain} = 101.76$$

$$(x) \text{ stage gm}_2 = 4.03 \times 10^{-4}$$

$$(xi) \text{ stage -2 gain} = 24.67$$

$$(xii) \text{ gm}_5 = 9.4 \times 10^{-5}$$

$$(xiii) \text{ overall gain} = 2510.61$$

$$(xiv) \text{ closed loop gain} = 2.124$$

Practical:

$$(i) \left(\frac{W}{L}\right)_7 = 3.77$$

$$(ii) \left(\frac{W}{L}\right)_0 = 38.88$$

$$(iii) \left(\frac{W}{L}\right)_1 = 30$$

$$(iv) \left(\frac{W}{L}\right)_2 = 30$$

$$(v) \left(\frac{W}{L}\right)_3 = 3.55$$

$$(vi) \left(\frac{W}{L}\right)_4 = 3.55$$

$$(vii) \left(\frac{W}{L}\right)_5 = 4$$

$$(viii) \left(\frac{W}{L}\right)_6 = 21.11$$

$$(ix) \text{ Stage -1 gain} = 101.2$$

$$(x) \text{ stage -2 gain} = 26.71$$

$$(xi) \text{ overall gain} = 2703.3$$

$$(xii) \text{ Phase margin} = 62^\circ$$

$$(xiii) \text{ Dominant pole} = 521295 \text{ s}^{-1}$$

$$(xiv) \text{ Power dissipation} = 128.86 \text{ pW}$$

$$(xv) \text{ closed loop gain (overall)} = 2.18$$

} open loop