

Design Assignment -2

This assignment has the maximum weightage among all the assignments

Design a 2-stage OTA in TSMC180nm technology.

TSMC 0.18 μ m technology parameters (taken from model file):

$V_{Tn} = 0.37\text{V}$; $V_{Tp} = 0.39\text{V}$; $\mu_n C_{ox} = 230 \mu\text{A/V}^2$; $\mu_p C_{ox} = 100 \mu\text{A/V}^2$; $V_{dd} = 1.8\text{V}$; $L_{min} = 0.18\mu\text{m}$; $W_{min} = 0.27\mu\text{m}$;

The designed opamp, should be used to make a non-inverting amplifier of gain 2 The DC gain of the opamp should be at least 40dB.

- The first part of your report should be your hand-design, and you should tabulate all calculated values as required in section
- Tabulate the following from your simulated design:
 - (a) W, L and operating points (g_m , r_o , $V_{GS} - V_T$, I_D) of all transistors. Use transistor names as follows: M_0 = input stage current source; M_{1-2} =input differential pair; M_{3-4} = current mirror active load; M_5 = second stage amplifier; M_6 =second stage current source.
 - (b)Values of other components in the opamp.
 - (c) DC gain of the opamp
 - (d) Power consumption
- Plot the transient response of the closed-loop amplifier with a 0.2V input step (use 0.1ns rise/fall times).
- Do not use an ideal current source in the tail. You can use one ideal reference current source of 1/10th the tail current of the input differential pair for bias generation
- You can assume a gate overdrive of 200mV in your initial calculations.
- Run a DC operating point simulation to get the small signal parameters from simulation. Adjust the bias currents/MOSFET sizes to get closer to the required parameters.
- You can also use the small signal parameters obtained from simulation to fine-tune the hand-calculated values, and get better estimates of other component values.